

Subject
Digital logic design

Project title
Bank vault laser alarm system

Group members
Abdullah (lead)
Wasay
Saim

- **circuit description**

This circuit is basically a security measure typically used to protect valuables in our case its a bank vault alarm system.

- **Logic explanation**

So whats happening in this circuit is, the arduino powers the breadboard which is housing the pir sensor working as a laser/motion detector when it detects motion it signals the piezo/ buzzer to go off indefinitely until you manually turn off the buzzer by clicking the alarm reset button

Side note the resistors are used to control the buzzer's intensity and limit the current so nothing receives too much power and burn

Pir sensor detected motion, the alarm will keep working until we manually press the reset button

